MYSTERY BOARDS

Draw lines to show how wires connect the brass fasteners.

A B

O O

C D





