


# Chapter 21

## Electric Current and Direct-Current Circuit


### Outline

- 21-1 Electric Current
- 21-2 Resistance and Ohm's Law
- 21-3 Energy and Power in Electric Circuit
- 21-4 Resistance in Series and Parallel
- 21-5 Kirchhoff's Rules
- 21-6 Circuits containing Capacitors
- 21-7 RC Circuits

**Figure 21-2**  
**The flashlight: A simple electrical circuit**

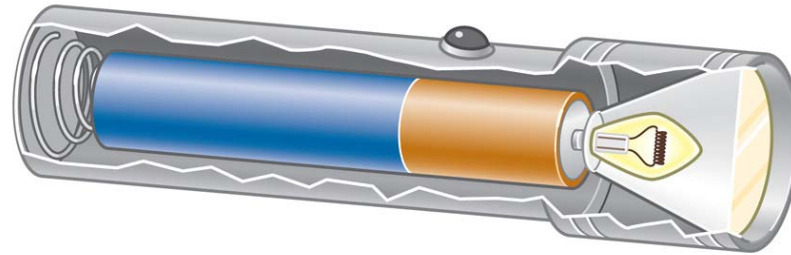

(a)

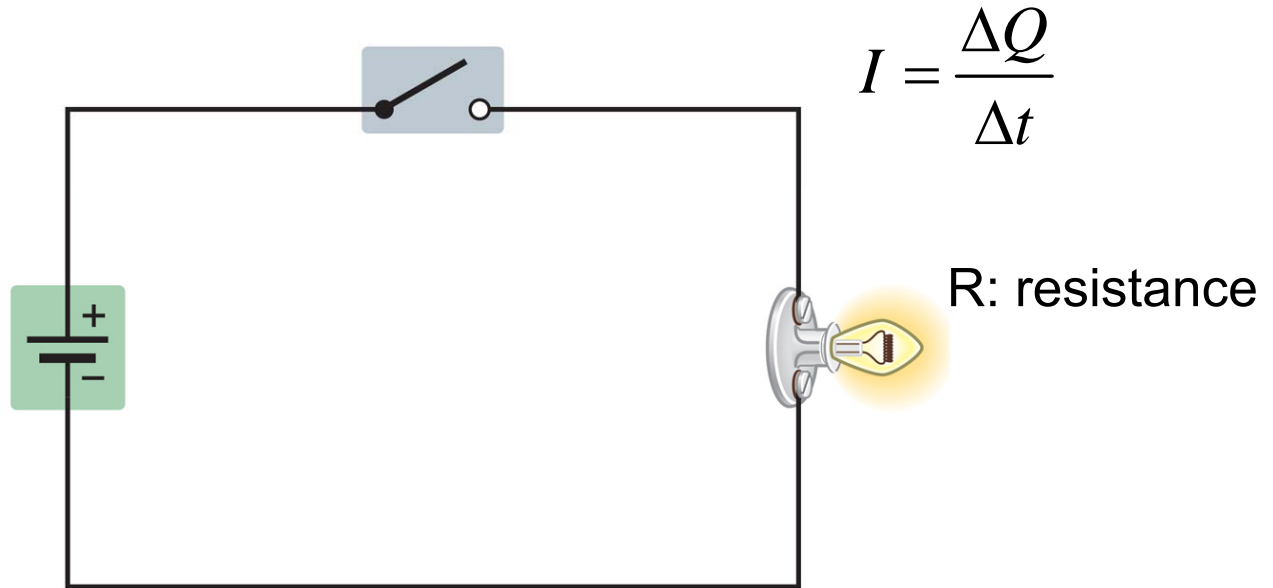

V: potential  
Difference/  
Voltage

$$I = \frac{\Delta Q}{\Delta t}$$

R: resistance

(b)

## 21-1 Electric Current

Definition of Electric Current,  $I$

$$I = \frac{\Delta Q}{\Delta t} \quad (21-1)$$

SI unit: Coulomb per second, C/s = Ampere, A

**Note:**


- 1) Electric current  $I$  is defined in a **Circuit/wire**.
- 2) Electric current  $I$  is independent to the time interval.

### 21-5 How Many Electrons


Highly sensitive ammeters can measure currents as small as  $10.0 \times 10^{-5}$  A. How many electrons in 2 seconds flow through a wire with  $10.0 \times 10^{-5}$  A current in this case?
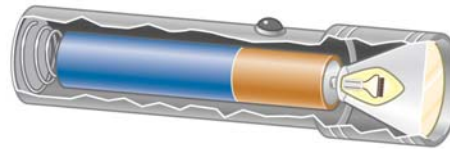
# Batteries and Electromotive Force

Electrons will move along a metal wire only when the wire is connected with a source of electric energy, such as a battery.



(a)

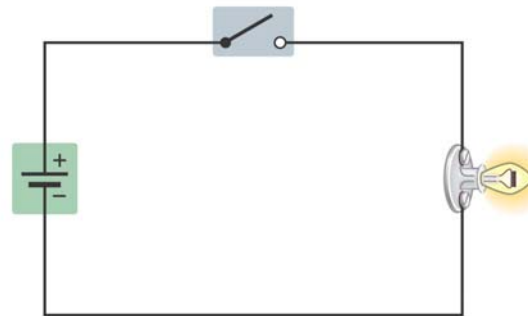

(b)

**Figure 21-2**  
**The Flashlight: A Simple Electrical Circuit**

The function of a battery is to provide an electric potential difference, so that the electric current (+ charges) can move in the wire.

The electric potential difference between its two terminals of the battery is referred as **Electromotive Force, or emf ( $\epsilon$ )**. The magnitude of the work done by a battery of emf  $\epsilon$  as a charge  $\Delta Q$  moves from one terminal to the other is given by Eq (20-2),

$$\epsilon = \frac{W}{\Delta Q}$$


$\epsilon$  Unit: volt, V

### Active Example 21-1

### Operating a Flashlight

A battery with an emf of 1.5 V delivers a current of 0.44 A to a bulb for 64 s (see Fig 21-2). Find **(a)** the charge that passes through the circuit and **(b)** the work done by the battery.

## The direction of the current in a circuit

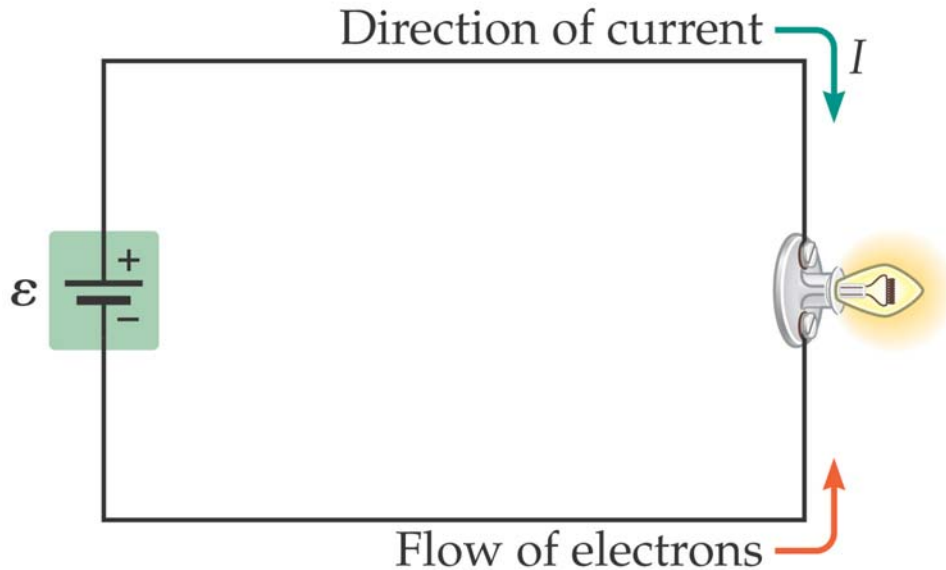

**Figure 21-4**  
**Direction of Current and Electron**  
**Flow**

The direction of the current in an electrical circuit is **the direction of the positive charge flowing**.



## 21-2 Resistance and Ohm's Law

In order to cause electrons to move against the resistance of a wire, one must apply a potential difference between its two ends. Assume  $R$  is the resistance,  $V$  is the potential difference, and the current is  $I$ ,

### Ohm's Law

$$V = IR$$

SI unit: volt, V

Solving for resistance:

$$R = \frac{V}{I}$$

SI unit:  $\Omega$ ,  $1\Omega = 1\text{ V} / \text{A}$

## 21-8 Resistance

When a potential difference of 18 V is applied to a given wire, it conducts 0.35 A of current. What is the resistance of the wire?

### Solution

With Ohm's law, one has

$$R = \frac{V}{I} = \frac{18 \text{ V}}{0.35 \text{ A}} = \boxed{51 \Omega}$$


# Resistivity

Suppose a piece of wire has length  $L$  and cross-section area  $A$ . The resistance of a material is determined by its resistivity  $\rho$ ,

Definition of Resistivity,  $\rho$

$$R = \rho \left( \frac{L}{A} \right) \quad (21-3)$$

Unit:  $\Omega \cdot \text{m}$

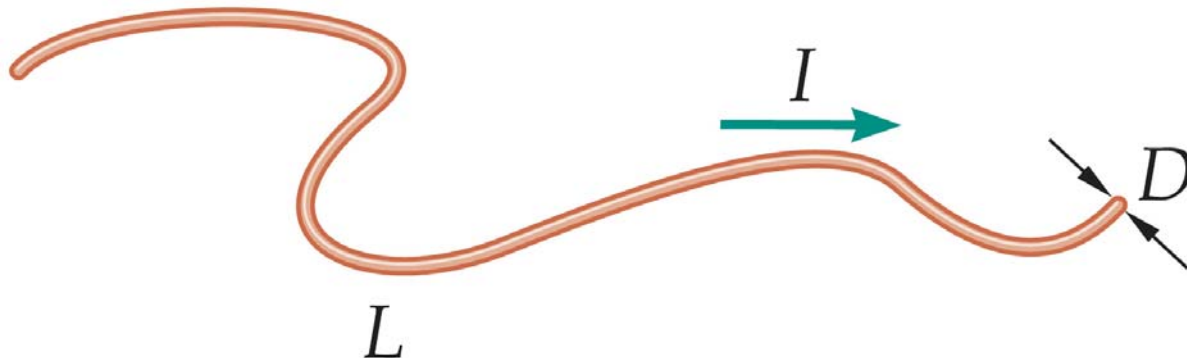

**Table 21-1  
Resistivities**

<b>Substance</b>	<b>Resistivity, <math>\rho</math> (<math>\Omega\cdot\text{m}</math>)</b>
------------------	--

---

**Insulators**

Quartz (fused)

$7.5 \times 10^{17}$

Rubber

1 to  $100 \times 10^{13}$

Glass

1 to  $10,000 \times 10^9$

**Semiconductors**

Silicon\*

0.10 to 60

Germanium\*

0.001 to 0.5

**Conductors**

Lead

$22 \times 10^{-8}$

Iron

$9.71 \times 10^{-8}$

Tungsten

$5.6 \times 10^{-8}$

Aluminum

$2.65 \times 10^{-8}$

Gold

$2.20 \times 10^{-8}$

Copper

$1.68 \times 10^{-8}$

Silver



$1.59 \times 10^{-8}$

\*The resistivity of a semiconductor varies greatly with the type and amount of impurities it contains. This property makes it particularly useful in electronic applications.

---
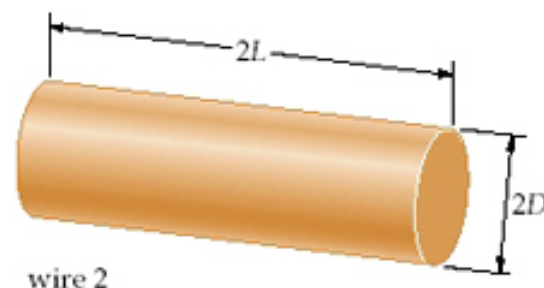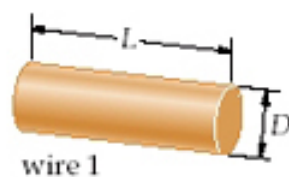
### CONCEPTUAL CHECKPOINT 21-1

Wire 1 has a length  $L$  and a circular cross section of diameter  $D$ . Wire 2 is constructed from the same material as wire 1 and has the same shape, but its length is  $2L$ , and its diameter is  $2D$ . Is the resistance of wire 2 (a) the same as that of wire 1, (b) twice that of wire 1, or (c) half that of wire 1?



**21-13 How long the wire is?**

A current of 0.76 A flows through a copper wire 0.44 mm in diameter when it is connected to a potential difference of 15 V. How long is the wire?

# Summary

## 1) Definition of Electric Current, $I$

$$I = \frac{\Delta Q}{\Delta t} \quad (21-1)$$

## 2) Ohm's Law

$$V = IR, \quad I = V / R$$

## 3) Definition of Resistivity, $\rho$

$$R = \rho \left( \frac{L}{A} \right) \quad (21-3)$$

### Example 21-1      Mega Blaster

The disk drive in a portable CD player is connected to a battery that supplies it with a current of 0.22 A. How many electrons pass through the drive in 4.5 s ?

#### Solution

1) Find the charge  $\Delta Q$ , according to the definition I

$$\Delta Q = I \times \Delta t = (0.22A)(4.5s) = 0.99C$$

2) Then find the number of electrons in charge  $\Delta Q$ ,

$$\begin{aligned} N &= \frac{\Delta Q}{e} = \frac{0.99C}{1.60 \times 10^{-19} C / \text{electron}} \\ &= 6.2 \times 10^{18} \text{ electrons} \end{aligned}$$



### Exercise 21-1

A potential difference of 24 V is applied to 150  $\Omega$  resistor. How much current flows through the resistance?


### Solution

With Ohm's law, one has

$$I = \frac{V}{R} = \frac{24V}{150\Omega} = 0.16 \text{ A}$$

### Examples 21-2 A current-Carrying Wire

A current of 1.82 A flows through a copper wire 1.75m long and 1.10 mm diameter. Find the potential difference between the ends of the wire. (the value  $\rho$  for copper is  $1.68 \times 10^{-8} \Omega \cdot \text{m}$ ).

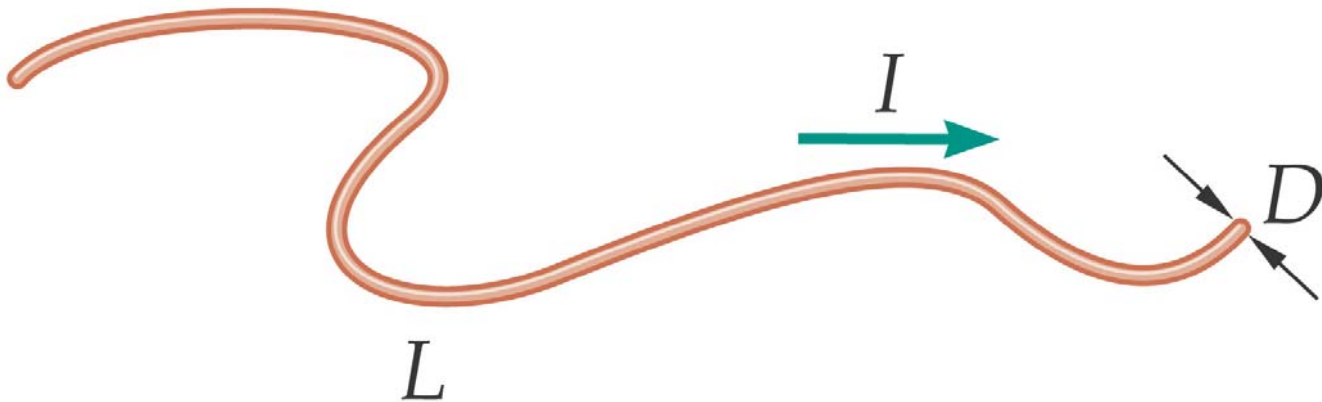

**Example 21-2**  
**A Current-Carrying Wire**

## Solution

1) Find the resistance of the wire

$$R = \rho \left( \frac{L}{A} \right) = (1.68 \times 10^{-8} \Omega \cdot m) \left[ \frac{1.75m}{\pi(0.00110m)^2 / 4} \right]$$
$$= 0.0309 \quad \Omega$$

2) Find the potential difference, according to Ohm's law

$$V = IR = (1.82 \text{ A}) (0.0309 \Omega) = 0.0562 \text{ V}$$